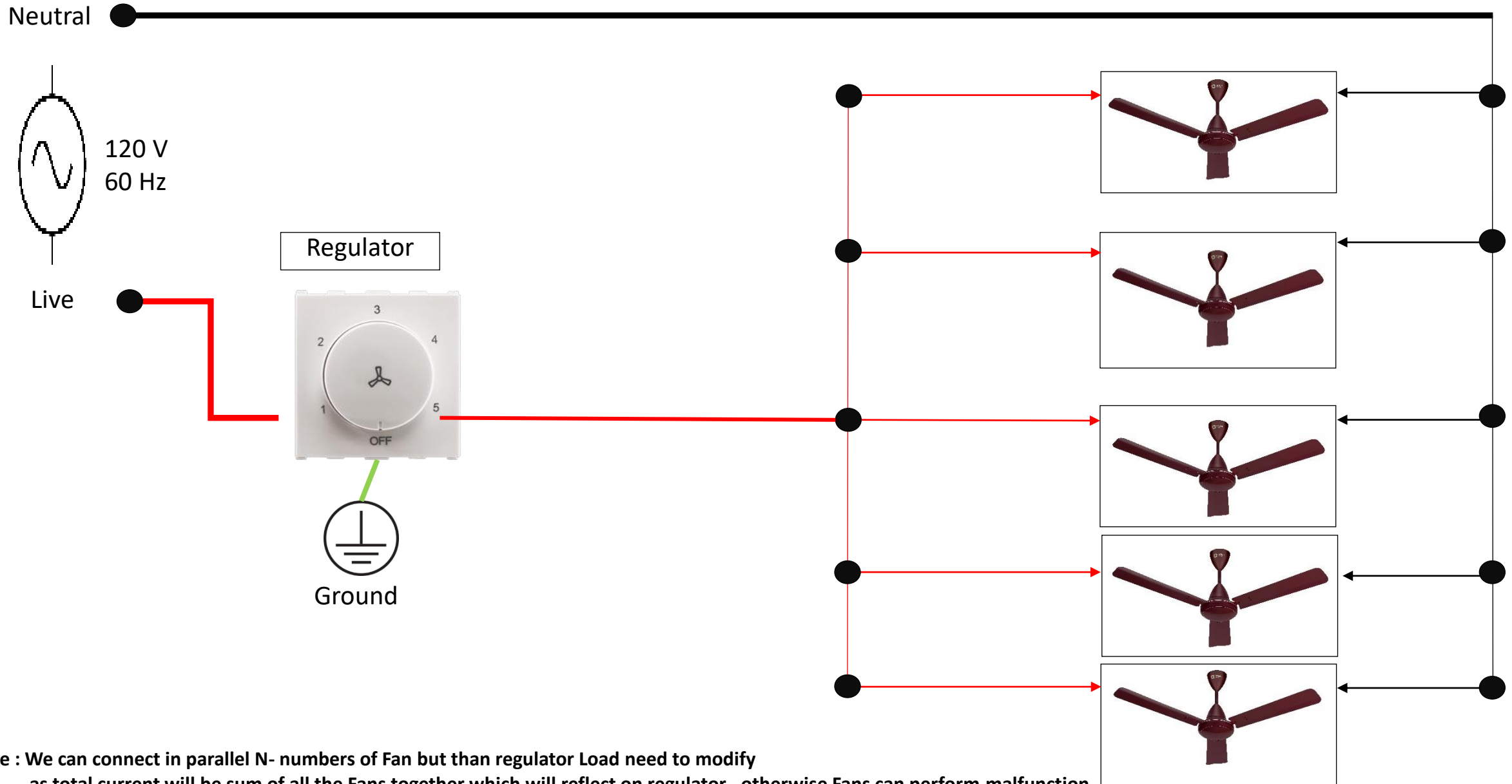


### Circuit diagram for connecting multiple fans with Regulator (Parallel Connection)



**Note :** We can connect in parallel N- numbers of Fan but than regulator Load need to modify as total current will be sum of all the Fans together which will reflect on regulator , otherwise Fans can perform malfunction.